

Lab 1: Diodes

Grabriel Ralph SID: 470205736

Liam Weichandt SID: 500463727


Part I

Looking at the graph we get


$a = (0.6V, 0.03mA)$, $b = (0.74V, 2.79mA)$. From the points the slope

$$m = \frac{\log_{10}(b_I) - \log_{10}(a_I)}{b_V - a_V} = 14.1$$

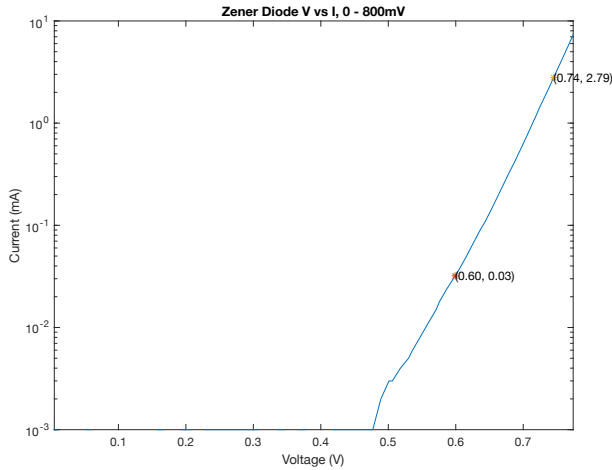was calculated. Hence for a $\times 10$ increase in current, voltage will increase by $\frac{1}{m} = 0.07V$. The slope seems to be equivalent to $\frac{1}{V_T}$ the thermal voltage.




It can be seen from the graph, breakdown starts at about $4.5V$ and occurs quite abruptly.

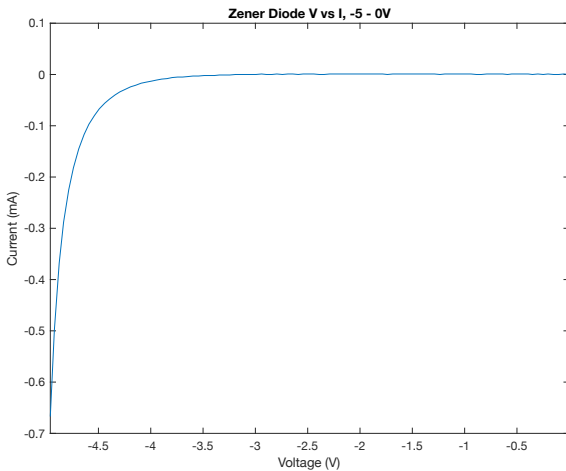

Part II

Led turn on voltage $1.4V$, as seen on graph.

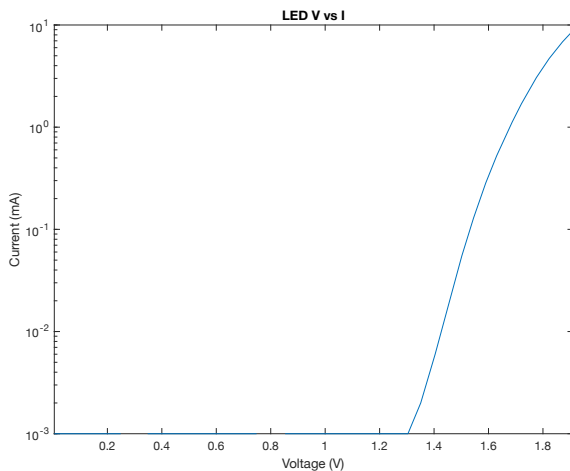

Part III

$$V_{max} = 551mV$$

$$V_{min} = 449mV$$


$$V_{discharge} = V_{min} + 0.367(V_{max} - V_{min})$$

$$V_{discharge} = 489mV$$

$$dt = 10^{-5}s \text{ (From measured data)}$$

$$RC = dt \text{ where } R = 100k\Omega$$

$$\therefore C = 100pF$$


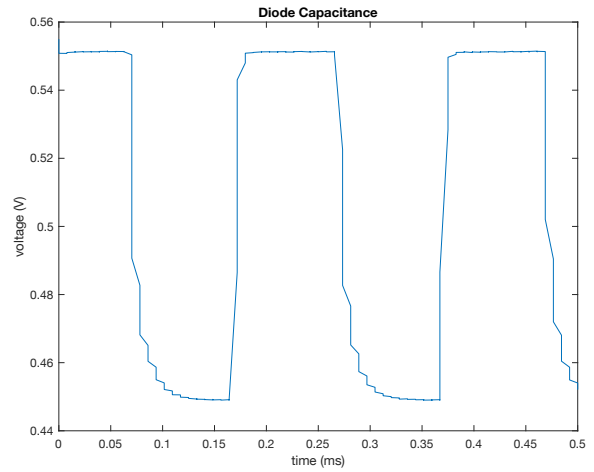


Part IV

$$V_{out} = 1.2V$$

$$dt_{out} = 56\mu s$$

The output waveform does not follow the input waveform as the output does not allow the negative portions of the input cycle to pass. This is because $IV_{in} < V_D$ which results in $V_{out} = 0$ for the negative cycle. Meaning the diode does not conduct. The flat portion of the waveform indicates this.

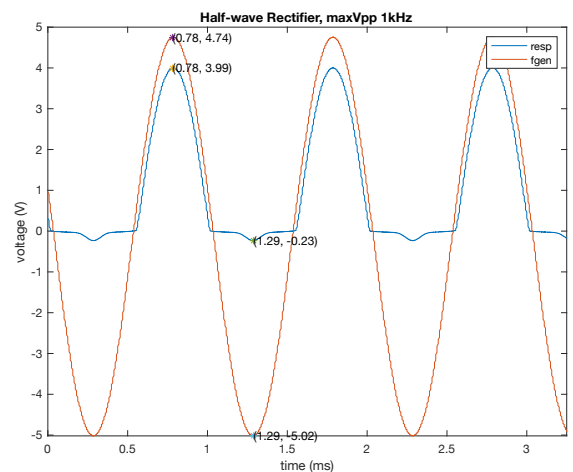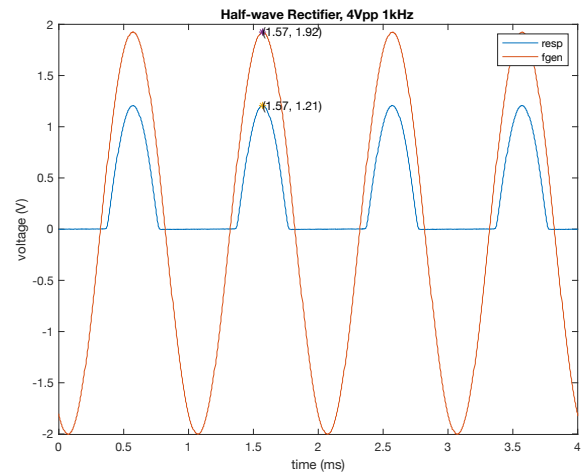

Part V

$$V_{in} > V_{breakdown}$$

$$V_D = V_{FGN} - V_R = V_{in} - V_{out} \\ = breakdown$$

As the diode is flipped from the previous questions, for the positive cycle, the diode is in reverse breakdown. However in the negative cycle, in order for the diode to conduct, $V_{in} > V_{turnon}$ is needed.

$$V_{in_{max}} = 9.1V$$

$$V_{out_{max}} = 3.9V$$

$$V_{in_{min}} = -9.5V$$

$$V_{out_{min}} = -8.5V$$

This gives a forward voltage drop of $V_D = 9.1 - 3.9 = 5.2V$.

