

# ELEC2104 – Lecture 08

## BJT Amplifiers, MOSFET



THE UNIVERSITY OF  
SYDNEY

## 4-resistor biasing: example


# Design of Four-Resistor Bias Network: Example

- Design 4-resistor bias circuit with given parameters:  $I_C = 750 \mu\text{A}$ ,  $\beta_F = 100$ ,  $V_{CC} = 15 \text{ V}$ ,  $V_{CE} = 5 \text{ V}$ . Assume we need to operate in forward-active region,  $V_{BE} = 0.7 \text{ V}$ 
  - Let  $V_E = 5 \text{ V}$ ,  $V_C = 10 \text{ V}$
  - Divide  $(V_{CC} - V_{CE})$  between  $R_E$  and  $R_C$ .

$$\alpha = \frac{\beta_F}{\beta_F + 1} = 0.99 \quad \longrightarrow \quad I_E = \frac{I_C}{\alpha} = 757 \mu\text{A}$$

$$R_E = \frac{V_E}{I_E} = 6.60 \text{ k}\Omega$$
 
$$R_C = \frac{V_{CC} - V_C}{I_C} = 6.67 \text{ k}\Omega$$



# Design of Four-Resistor Bias Network: Example


- Design 4-resistor bias circuit with given parameters:  $I_C = 750 \mu\text{A}$ ,  $\beta_F = 100$ ,  $V_{CC} = 15 \text{ V}$ ,  $V_{CE} = 5 \text{ V}$ . Assume we need to operate in forward-active region,  $V_{BE} = 0.7 \text{ V}$ 
  - Set  $I_1 = 10I_B$  and  $I_2 = 9I_B$

$$I_B = \frac{I_C}{\beta_F} = 7.5 \mu\text{A}$$

$$V_B = V_E + V_{BE} = 5.7 \text{ V}$$

$$I_1 = 10I_B = 75 \mu\text{A} \longrightarrow R_2 = \frac{V_B}{I_2} = 84.4 \text{ k}\Omega$$

 
$$I_2 = 9I_B = 67.5 \mu\text{A} \longrightarrow R_1 = \frac{V_{CC} - V_B}{I_1} = 124 \text{ k}\Omega$$



# Two-resistor biasing
 
# Two-resistor biasing (with collector-to-base feedback resistor)

- We can self-bias a transistor to force it into forward-active operation (guaranteed)
  - With  $R_B$ , the collector must be at a higher potential than the base
  - If BE junction is off (hence BJT is in cutoff), then  $V_X = V_Y = V_{CC}$ , hence  $V_{BE} = V_X > V_{on}$
  - The transistor hence must be in forward-active operation.
- The collector voltage provides the necessary  $V_X$  and  $I_B$ .



$$V_Y = V_{CC} - I_E R_C = V_{CC} - I_C (1 + 1/\beta) R_C$$
$$V_Y = I_B R_B + V_{BE} = \frac{R_B I_C}{\beta} + V_{BE}$$

$$\Rightarrow I_C = \frac{V_{CC} - V_{BE}}{(1 + 1/\beta) R_C + R_B/\beta}$$


$$R_C \gg \frac{R_B}{\beta}$$

provides insensitivity of Q-point ( $I_C$ ) to  $\beta$

$$\Delta V_{BE} \ll V_{CC} - V_{BE} \quad \text{provides insensitivity of Q-point } (I_C) \text{ to variation in } \Delta V_{BE}$$
 
# Two-Resistor Bias Network Analysis: Example

- Find Q-point for pnp transistor in a two-resistor bias circuit with  $\beta_F = 50$ ,  $V_{CC} = 9\text{ V}$ . Assume it is in forward-active operation, so  $V_{EB} = 0.7\text{ V}$ .



Analysis is the same as for a npn transistor

Apply Kirchoff's Voltage Law:


$$-V_{CC} + V_{EB} + V_{BC} + V_C = 0$$

$$V_{EB} + 18\,000I_B + 1000(I_C + I_B) = 9$$

$$V_{EB} + 18\,000I_B + 1000(51)I_B = 9$$
 
# Two-Resistor Bias Network Analysis: Example

- Find Q-point for pnp transistor in a two-resistor bias circuit with  $\beta_F = 50$ ,  $V_{CC} = 9\text{ V}$ . Assume it is in forward-active operation, so  $V_{EB} = 0.7\text{ V}$ .



$$V_{EB} + 18\,000I_B + 1000(51)I_B = 9$$

$$I_B = \frac{9\text{ V} - 0.7\text{ V}}{69\,000\,\Omega} = 120\,\mu\text{A}$$


$$I_C = 50I_B = 6.01\text{ mA}$$

$$V_{EC} = 9 - 1000(I_C + I_B) = 2.88\text{ V}$$


**Q-point is : (6.01 mA, 2.88 V)**





# Summary of Biasing Techniques

 

Sensitive  
to  $\beta$

 


Sensitive  
to Resistor Error

  

Always in  
Active Mode

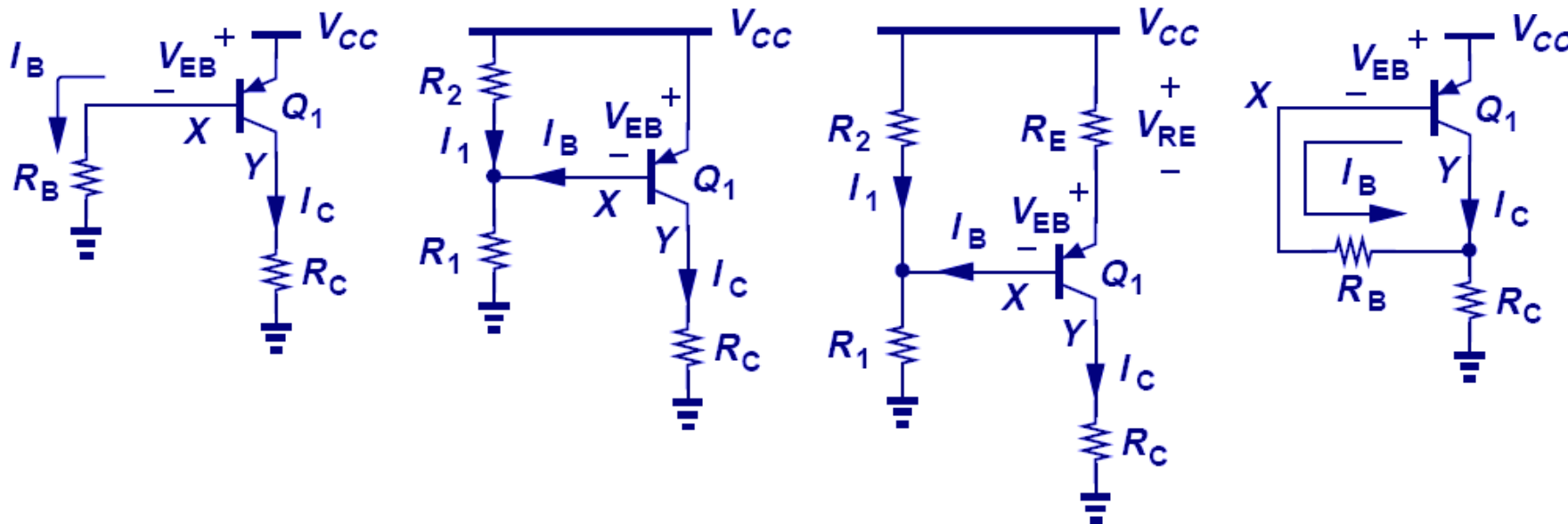
# PNP Transistor Biasing

- Exact same principles, exact same design techniques
- Pay attention to direction of voltage and current




# BJT amplifier topologies


# BJT Amplifier Topologies

 

Common-Emitter

 

Common-Base

 


Emitter-Follower

- These are the most useful configurations
- All of  $v_{out}$ ,  $v_{in}$  are small signals (on top of  $V_C$ ,  $V_B$  etc.). Assuming we have biased the BJT correctly.

# Common-Emitter Amplifier


- Gain of amplifier – Voltage gain

 

$$A_V = \frac{v_{out}}{v_{in}}$$

$$-\frac{v_{out}}{R_C} = g_m v_\pi = g_m v_{in}$$
 
$$r_\pi = \frac{\beta}{g_m} \quad g_m = \frac{I_C}{V_T}$$




$$A_V = -g_m R_C$$

# Common-Emitter Amplifier


- Input/Output Impedance
  - Determines the capability to interface with preceding and following stages
  - When measuring the output impedance, the input port has to be grounded so that  $V_{in}$  is grounded, i.e. we don't care whatever circuit was connected to B. (again, this is the small signal circuit)

Input Impedance  
(Ideally infinite)

 

$$R_{in} = \frac{v_x}{i_x} = r_\pi = \frac{\beta V_T}{I_C}$$

Output Impedance  
(Ideally zero)

 


$$R_{out} = \frac{v_x}{i_x} = R_C \quad (\text{since } v_\pi = 0)$$

Tradeoff between output  
impedance and voltage gain
 
# Common-Emitter Amplifier with Early effect

- Early effect will lower the gain of the CE amplifier, as it appears in parallel with  $R_C$ .



$$r_o = \frac{V_A}{I_C}$$


$V_A$ : Early voltage

$$A_V = -g_m(R_C || r_o)$$

$$R_{out} = R_C || r_o$$
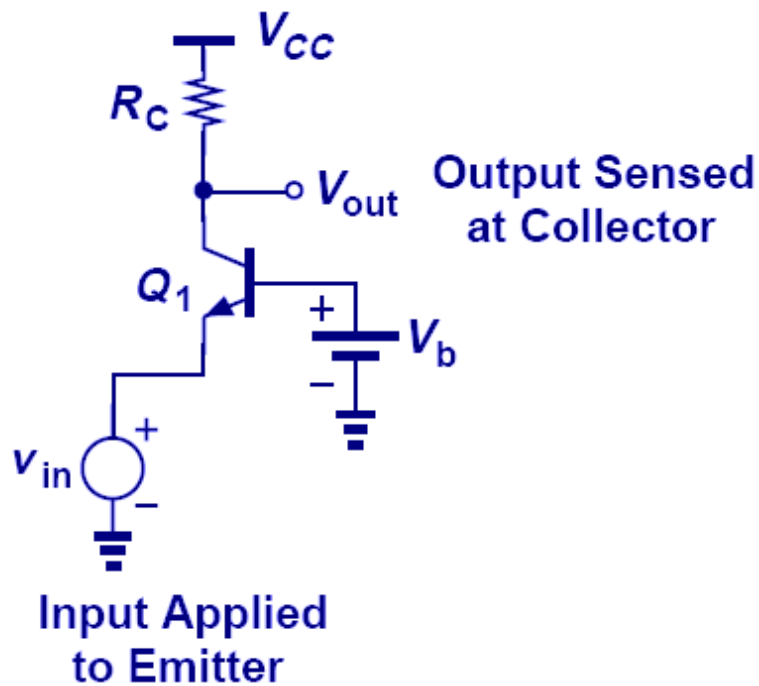
# Common-Base Amplifier

- In common base topology, where the base terminal is biased with a fixed voltage, emitter is fed with a signal, and collector is the output.





Why does this work?

Change in  $V_E$  changes  $V_{BE}$ , hence  $I_C$


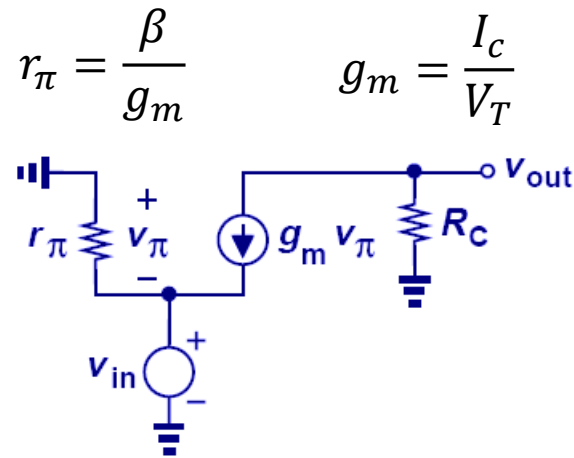 
# Common-Base Amplifier

- Voltage gain
  - The voltage gain of CB stage is  $g_m R_C$ , which is identical to that of CE stage in magnitude and opposite in phase (positive  $V_{in}$  means negative  $V_{BE}$ ).





$$A_V = \frac{v_{out}}{v_{in}}$$

$$v_\pi = -v_{in} \quad -\frac{v_{out}}{R_C} = g_m v_\pi = -g_m v_{in}$$

$$A_V = g_m R_C$$
  
# Common-Base Amplifier

- The input impedance of CB stage is much smaller than that of the CE stage.



$$i_x = -\left(g_m v_\pi + \frac{v_\pi}{r_\pi}\right)$$

$$v_\pi = -v_{in}$$



$$R_{in} = \frac{1}{g_m}$$

$$(R_{in} = r_\pi = \frac{\beta}{g_m} \text{ for CE})$$

- CB stage's low input impedance can be used to create a match with 50  $\Omega$  transmission line (no reflection to the transmission line)

- However, low input impedance could mean input signal is attenuated

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}}$$


$v_{sig}$ : incoming signal

$v_{in}$ : input received by the circuit

$R_{sig}$ : impedance of the signal (output impedance from previous stage)



- Output impedance:

- Same as CE stage

 
  
# BJT Amplifier: Example

- The circuit below is biased with a collector current of 1 mA and  $R_C = 1\text{ k}\Omega$ . If  $\beta = 100$ ,  $V_T = 26\text{ mV}$ , and  $V_A = 10\text{ V}$ , determine the small-signal voltage gain and the I/O impedances.



Early effect reduces the voltage gain

$$g_m = \frac{I_c}{V_T} = \frac{1 \times 10^{-3}}{26 \times 10^{-3}} = (26\ \Omega)^{-1}$$

$$r_\pi = \frac{\beta}{g_m} = 100(26) = 2.6\text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{10\text{ V}}{1\text{ mA}} = 10\text{ k}\Omega$$

$$A_V = -g_m(R_C || r_o)$$

$$= -\frac{1}{26} (1\text{ k}\Omega || 10\text{ k}\Omega) \approx -35 \quad \text{If no early effect: } A_V \approx -38$$


$$R_{in} = r_\pi = 2.6\text{ k}\Omega$$

$$R_{out} = (R_C || r_o) = 909\ \Omega$$

# Recap

- P-type and N-type semiconductors

Drift Current

 

$$J_n = q n \mu_n E$$

$$J_p = q p \mu_p E$$


Diffusion Current




$$J_n = q D_n \frac{dn}{dx}$$

$$J_p = -q D_p \frac{dp}{dx}$$


- PN Junctions as Diodes

 

Depletion Region

 




Forward bias

 



Reverse bias

# Recap

- Diode Models

   

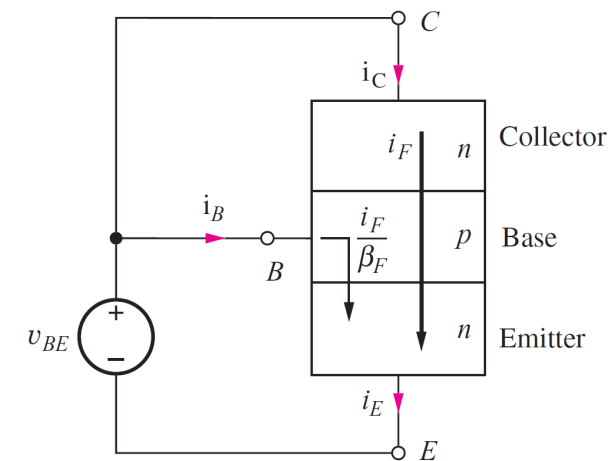 - Append two PN junctions together to create BJT



**Active mode of operation**

# ELEC2104 – Week 8: Part II

## MOSFET – Theory of Operation




**Textbook Chapter Reading:**  
**Chapter 4.1 – 4.4**



THE UNIVERSITY OF  
**SYDNEY**
 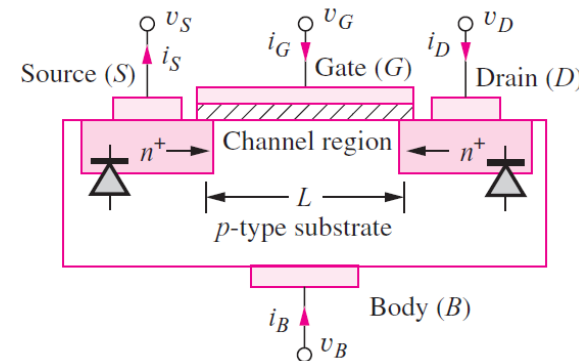 
# Metal-Oxide Semiconductor




- **MOSFET:** Metal-oxide-semiconductor Field Effect Transistor
- **Four** terminals device
- **Gate (G):** Top conductive plate (e.g. metal) residing on a thin dielectric (oxide insulator) layer
- Two heavily doped regions ( $n^+$  or  $p^+$  type):
  - **Source (S)** – provides carriers
  - **Drain (D)** – receive carriers
- **Substrate or Body:** p- or n-type semiconductor
  - NMOS or PMOS transistors
    - NMOS: electrons flow in the channel



$i_G$  usually 0
   
# MOS Capacitor Operation




- First, understand the MOS operation
- Consider a simple geometry consisting of a conductive plate (**M**etal), an insulator (**O**xide insulator) and a lightly doped piece of silicon (**S**emiconductor)
- Apply  $V_1$  on the top plate
  - Attracts negative charges (electrons)
  - Creates a channel of free electrons
$$Q = CV_1$$
  - Forms a good conductive path with least resistance
- Apply  $V_2$  across the silicon
  - Electrons drift from left to right
  - Current flows through the channel





   
# MOSFET Structure

- N-type MOS (NMOS) Transistor
- Central region is the MOS cap
- N-type source/drain and p-type substrate
- Two n-well regions on either side of the MOS capacitor can supply electrons
  - Symmetric. Unlike BJT



 
# N MOSFET Operation

- First, consider the arrangement where:
  - Source (S) and Drain (D) are grounded
  - Gate (G) voltage is near zero
  - No current can flow



 
# N MOSFET Operation

- $V_{GS} < V_{TN}$ 
  - As  $V_G$  rises, positive charge on the gate repels the holes in the substrate, exposes negative ions, and creates depletion region
  - Depletion region is devoid of free carriers,
  - No channel of mobile charges formed yet, still no current



 
# N MOSFET Operation

- $V_{GS} > V_{TN}$ 
  - $V_G$  becomes sufficiently positive, free electrons are attracted to the oxide-silicon interface
  - An inversion layer is formed, a conductive channel connecting S to D
  - The voltage at which this layer just forms -> “threshold voltage”  $V_{TN}$


 
# N MOSFET Operation


- The conductive channel between S and D can be viewed as a voltage-dependent resistor




Now, with a voltage applied  
between S and D, current can flow.
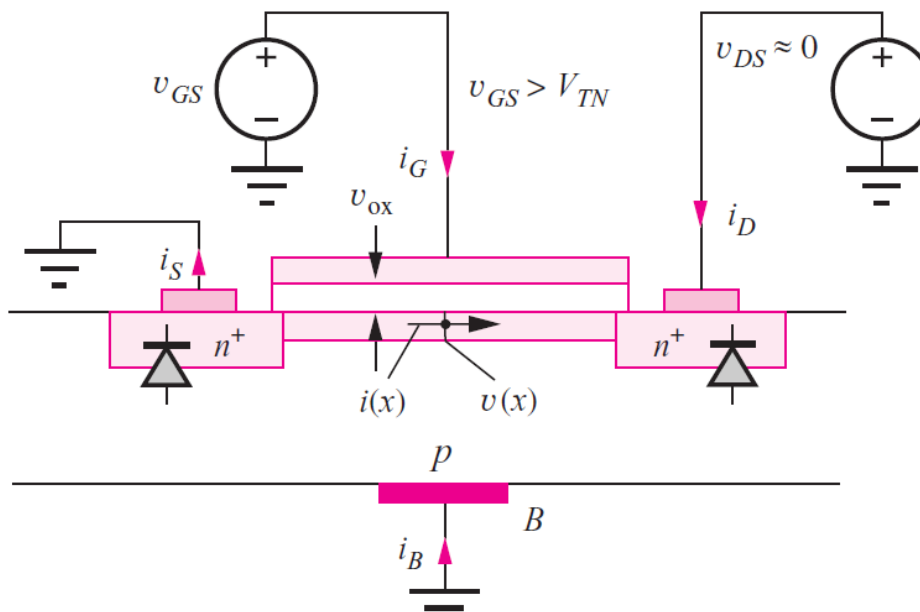
# N MOSFET Operation

- If positive voltage is applied between D and S, electrons in the channel inversion layer will flow  $\rightarrow I_D > 0$
- Gate terminal is insulated from the channel,  $i_G = 0$ .





 What is the current transport mechanism in a MOSFET?  
Drift.



 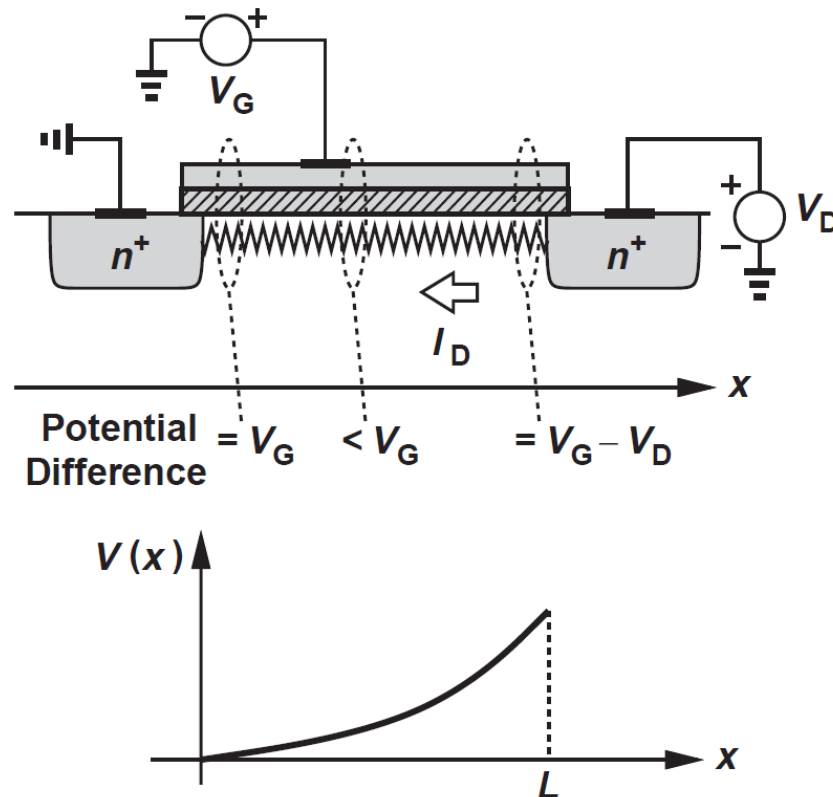
# Channel Pinch-Off

- If the drain voltage ( $V_D$ ) remains higher than source voltage ( $V_S$ ), the voltage at each point along the channel with respect to ground increases as we go from S to D
- Potential difference between gate and substrate is reduced close to drain
- Density of electrons falls to minimum at  $x = L$ .


 
# Channel Pinch-Off


- If  $V_D$  is high enough,  $V_G - V_D \leq V_{TN}$ , the channel ceases to exist near the drain.
  - Gate-substrate potential difference is not sufficient to attract electrons
- Channel is pinched off




 
# Channel Pinch-Off



- If  $V_D$  rises further,  $V_D > V_G - V_{TN}$  at  $x = L$
- Voltage difference between gate and substrate falls to  $V_{TN}$  at  $L_1 < L$
- Device contains no channel between  $L_1$  and  $L$ .



Can the device still conduct?

  
# Channel Pinch-Off

- The end of the channel at  $L_1$  is in the depletion region.
- Electrons are rapidly swept to D due to the built-in E field in depletion region.
- When  $V_D > V_G - V_{TN}$ ,  $V_D$  no longer affects current significantly
- MOSFET acts as a constant current source independent of  $V_{DS}$




Electrons injected into depleted region gets swept onto the drain

 
# Channel pinch-off (with depletion region shown)



(a)  $V_G > V_T$ ,  $V_D \approx 0$

 


(b)  $V_G > V_T$ ,  $V_D < V_G - V_T$

 

(c)  $V_G > V_T$ ,  $V_D > V_G - V_T$
 
# Channel current related to channel charge



Starting out with  $Q = CV$ , as channel voltage varies along  $x$ :

$Q$ : charge density in the channel per area  
 $W$ : width of the channel  
 $C_{ox}$ : capacitance in the oxide per area

$$Q(x) = C_{ox}(V_{GS} - V_{TN} - V(x))$$

$$I_{drift} = -WQ(x)\mu_n E = WQ(x)\mu_n \frac{dV}{dx}$$

$$\begin{aligned} \int_0^L I_D dx &= WC_{ox}\mu_n \int_{V_S}^{V_D} (V_{GS} - V_{TN} - V(x)) dV \\ &= WC_{ox}\mu_n \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} \end{aligned}$$

On the other hand,  $I_D$  should be constant because of current conservation, hence  $\int_0^L I_D dx = I_D L$

$$I_D = \beta \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = \frac{1}{2} \beta [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$\text{where } \beta = \mu_n C_{ox} \frac{W}{L}$$


# MOSFET Regions of operations

# Regions of Operations

- Linear or Triode Region

$$V_{GS} - V(x) \geq V_{TN} \text{ for } 0 \leq x \leq L$$

 - Resistive channel directly connects the source and drain



$$I_{D,\text{tri}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

- For small drain voltages:  $\frac{V_{DS}}{2} \ll (V_{GS} - V_{TN})$

$$I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN}) V_{DS}$$



Acts like a resistor connected between drain and source

# On Resistance

- Resistor value can be controlled by the gate-source voltage

$$R_{on} = \frac{V_{DS}}{I_D} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})}$$

  
- Near the origin, the i-v curves can be approximated by straight lines having different slopes




 
# Regions of Operations

- Saturation Region

- Drain current saturates at a constant value for  $V_{DS} > V_{GS} - V_{TN}$



Pinch-off:  $V_{DS} = V_{GS} - V_{TN}$

  



$$\int_0^{L_1} I_D dx = \int_{V_S}^{V_{GS}-V_{TN}} W C_{ox} \mu_n (V_{GS} - V(x) - V_{TN}) dV$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_1} (V_{GS} - V_{TN})^2 \quad \text{Independent of } V_{DS}$$




# Regions of Operations

- Linear/Triode and Saturation Regions

  
 
# Determining Region of Operation



- What region of operation is this transistor operating in?
- Circuit analysis is much easier than with BJTs, because current can only go in one direction
- For the example below, it's triode or saturation: plug numbers into equations to verify


  
# MOSFET Regions Of Operation



- NMOS:

- Cut-off ::  $V_{GS} = 0$
- Saturation ::  $V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$
- Triode ::  $V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$



- For PMOS, all values are negative:

  - Cut-off ::  $V_{GS} = 0$
- Saturation ::  $V_{GS} < V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$
- Triode ::  $V_{GS} < V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$



- Equations end up being the same

$$I_{D,sat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$I_{D,tri} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

# Bipolar Transistor versus MOSFET Summary

- Comparison of Bipolar Transistor and MOSFET characteristics:


Bipolar Transistor	MOSFET
<b>Exponential Characteristic</b> Active: $V_{CB} > 0$ Saturation: $V_{CB} < 0$ Finite Base Current Early Effect Diffusion Current –	<b>Quadratic Characteristic</b> Saturation: $V_{DS} > V_{GS} - V_{TH}$ Triode: $V_{DS} < V_{GS} - V_{TH}$ Zero Gate Current Channel-Length Modulation Drift Current Voltage-Dependent Resistor

- Bipolar devices have a higher  $g_m$  than MOSFETs for a given bias current due to its exponential IV characteristics

# MOSFET channel-length modulation

 
# Channel-Length Modulation

- Drain current is not quite constant in the saturation region
- Drain current does increase slightly as drain-source voltage increase



$$L = L_M - \Delta L$$


 
Actual length  $L$  of resistive channel decreases as  $\Delta L$  increases with  $V_{DS}$



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_1} (V_{GS} - V_{TN})^2 \quad \Rightarrow \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad \lambda: \text{Channel-length modulation parameter}$$
  
# Channel Length Modulation

- Unlike the Early voltage in BJT, the channel-length modulation factor can be controlled by the circuit designer.
  - We cannot control base width in a BJT, but we can control gate length of a MOSFET
  - For long  $L$ , the channel-length modulation effect is less than that of short  $L$ .




Body effect


 
# Body Effect in Strong Inversion


- So far, we have assumed both source and substrate are tied to ground.
- What happens if the substrate is at a different voltage from the source?
- Threshold voltage can change:  $V_{Th} = V_{Th0} + \gamma(\sqrt{V_{SB} + 2\psi_B} - \sqrt{2\psi_B})$



$V_{Th0}$  = threshold voltage for  $V_{SB} = 0$

$$\gamma = \text{body-effect parameter} = \frac{\sqrt{qN_A 2\epsilon_s}}{C_{ox}} \quad (\sqrt{V})$$


$2\psi_B$  = surface potential (V)

 
 
# Body Effect

- For most circuits in this course, the substrate will be connected to the same potential as the source.
- Then, no effect.


$$V_{Th} = V_{Th0} + \gamma(\sqrt{V_{SB}} + 2\psi_B - \sqrt{2\psi_B})$$



# MOSFET circuit models
 
# MOSFET Circuit Models


- A MOSFET can be represented using different circuit models depending on its region of operation
- When it is operating in the triode region, but  $V_{DS}$  is much smaller than  $(V_{GS} - V_{Th})$ , the I-V curve is linear
- The MOSFET is a resistor independent of  $V_{DS}$



$$I_{D,tri} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$
$$\approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})V_{DS}$$

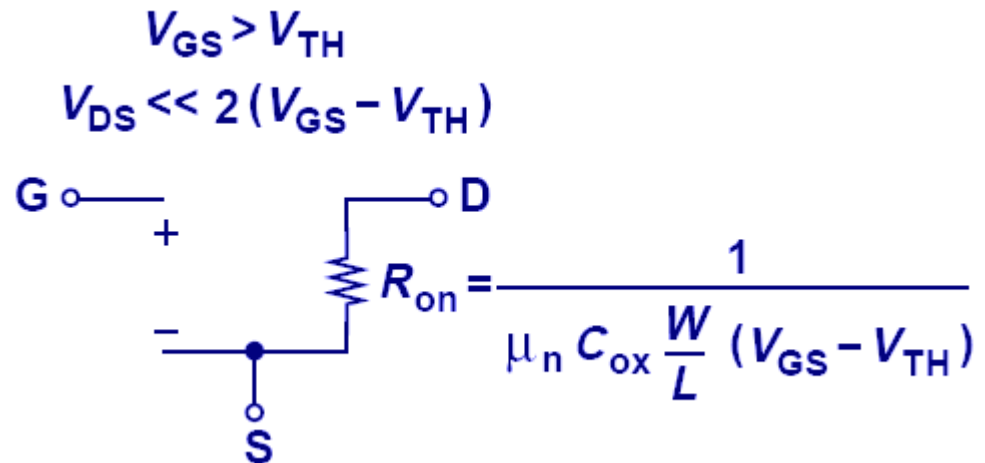
# Linear Triode Circuit Model

- When it is operating in the triode region, but  $V_{DS}$  is much smaller than  $(V_{GS} - V_{TH})$ , the I-V curve is linear




$$I_{D,tri} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN}) V_{DS}$$
 
$$R_{on} = \frac{V_{DS}}{I_D} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})}$$



 
# Triode Operation

- This type of gain control finds application in cell phones to avoid saturation near base stations


 
# Non-linear Triode Circuit Model


- When operating in the triode region, and  $V_{DS}$  approaches  $(V_{GS} - V_{Th})$ , the I-V curve is non-linear
- The MOSFET is a voltage-controlled current source.



$$I_{D,\text{tri}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$
 
# Non-linear Triode Circuit Model


- When operating in the triode region, and  $V_{DS}$  approaches  $(V_{GS} - V_{TH})$ , the I-V curve is non-linear
- The MOSFET is a voltage-controlled current source.




 
# Saturation Circuit Model


- When operating in saturation,  $V_{GS} > V_{TH}$  and  $V_{DS} > V_{GS} - V_{TH}$
- Ideally the drain current would be only dependent on  $V_{GS}$
- If we want to take channel-length modulation into account, it must be a voltage-controlled current source as well



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

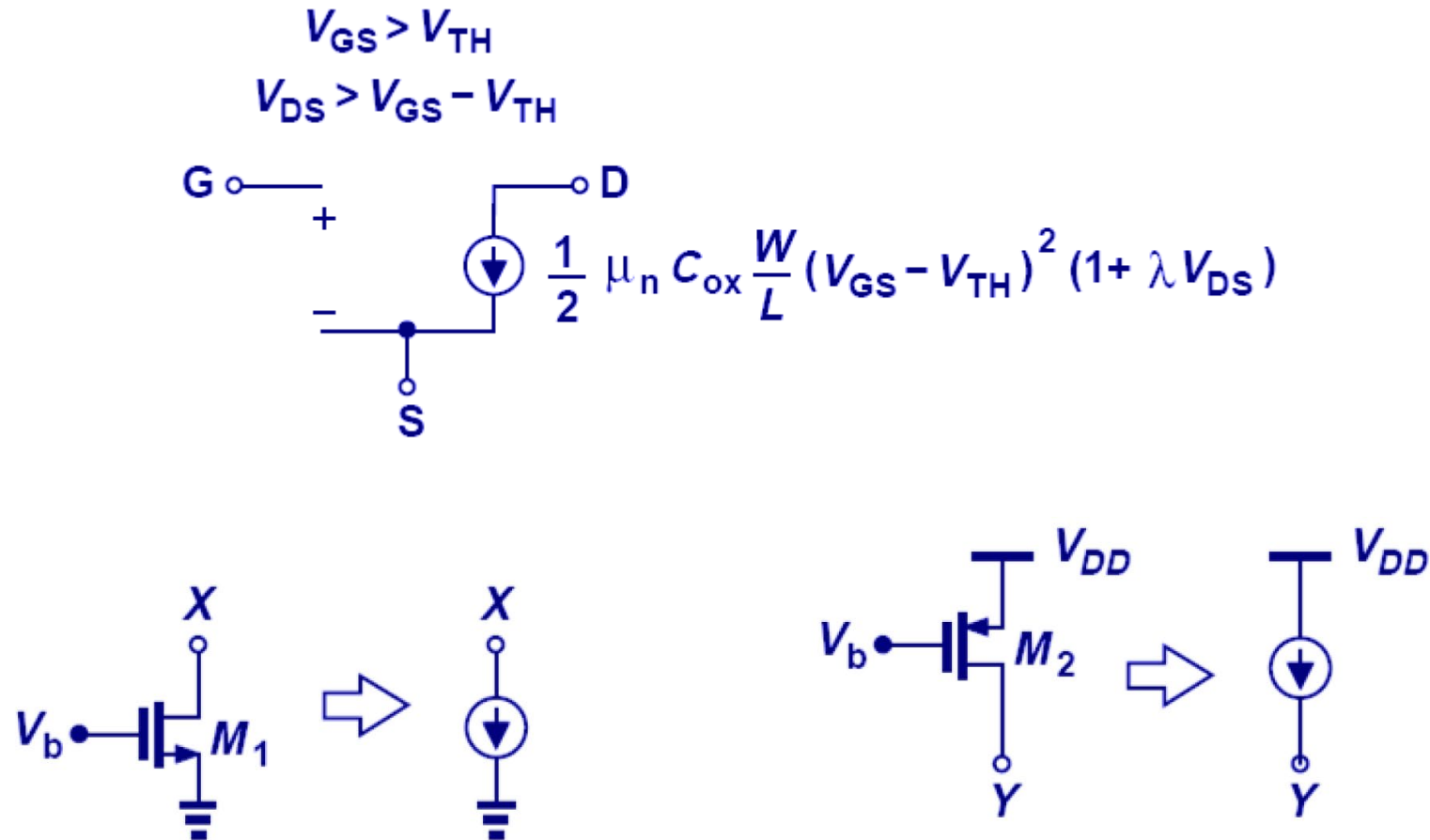
# Saturation Circuit Model

- The MOSFET in saturation is a voltage-controlled current source




# Backup slides - MOSFET


# Inversion Channel And Gate Voltage

 

# Inversion Channel And Gate Voltage

 


# Inversion Channel at Threshold

 


$V_G = V_{Th} \Rightarrow \text{\#electrons} = \text{\#holes in the channel}$

# Inversion Channel

 
 
# Channel Current

- $V_{DS} > 0$ , potential at oxide silicon interface rises from S to D
- Potential difference between gate and oxide silicon interface decreases as it approaches the drain ( $V_{GS} - V_{DS}$ ), electron density decreases accordingly





# Channel Pinch-Off

- At  $V_{GS} - V_{DS} \leq V_{TN}$  -> channel ceases to exist
- Pinch-off voltage:  $V_P = V_{GS} - V_{TN}$

